

Analog Electronic Circuits (EC2.103) : Quiz-2

Instructor: Prof. Abhishek Srivastava, CVEST, IIIT Hyderabad

Date : 19th May, 2023, Duration : 45 minutes, Max. Marks : 10

Instructions:

- Clearly write your valid assumptions (if any)
- You are only allowed to use own handwritten single A-4 sheet (both sides) as short notes
- Mobile phone, computers can not be used during the exam

1. As shown in figure 1, derive the expression for small signal input resistance R_{in} and fill in the blanks. Consider that both transistors (Q_1 & Q_2) are in active mode and symbols have their usual meanings. (Hint: Draw small signal equivalent, apply v_{in} , measure i_{in} , then $R_{in} = \frac{v_{in}}{i_{in}}$) [4 Mark]

$$R_{in} = (---)r_{\pi 1} + (---)r_{\pi 2} + (---)R_E$$

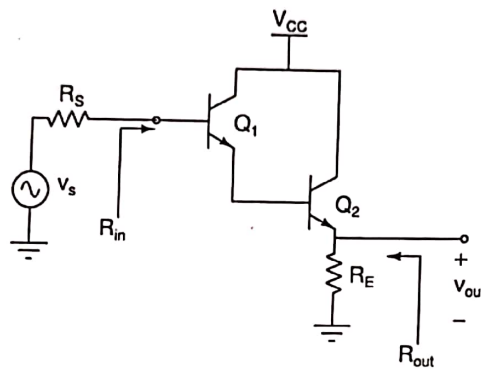


Figure 1

2. For the amplifier topology shown in figure 2, it is given that $\beta = 100$, $I_S = 6 \times 10^{-16}$ A and $V_A = \infty$.

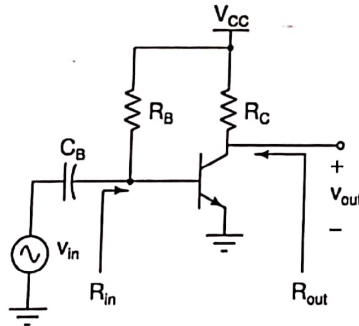


Figure 2

- (a) Draw small signal equivalent and derive voltage gain ($A_v = \frac{v_{out}}{v_{in}}$). [1 Mark]
- (b) Derive the expressions for R_{in} and R_{out} . [1 Mark]
- (c) Design the amplifier to achieve following specifications: $A_v \geq 8$, $R_{out} = 1 \text{ k}\Omega$, $R_{in} \geq 5 \text{ k}\Omega$, $V_{CC} = 2.5 \text{ V}$, lowest signal frequency of interest ($f_{in_{min}}$) is 100 Hz and overall power dissipation $P_{DC} \leq 1 \text{ mW}$. Tabulate the final design parameters (A_v , R_{in} , R_{out} , P_{DC}) achieved in your design. (Hint: Design means you need to find R_C , R_B & C_B values to satisfy the requirements. $I_C = I_S \exp(\frac{V_{BE}}{V_T})$, $I_C = \beta I_B$) [4 Mark]

Good luck !!