

## DFT Quiz -1

27<sup>th</sup> August 2024

Total: 40 Marks  
Duration: 45 minutes

### Instructions:

- This is a closed book exam.
- Answer legibly. Answer all parts of a question contiguously.
- If you have to make any assumptions, state those assumptions clearly. Points awarded will depend on the nature of the assumptions.

1. Answer the following questions:
  - a. Differentiate between Verification, Validation and Testing. (3 Marks)
  - b. Explain the difference between characterization test and production test. (2 Marks)
  - c. State the main assumptions in the Single Stuck at Fault Model. (3 marks)
  - d. How do we test for reliability in integrated circuits? (2 Marks)
  - e. Differentiate between functional and structural faults. (2 Marks)
  - f. Which fault would be best detected using IDDQ testing? (1 Mark)
  - g. Which fault model is best suitable for testing a critical path in a high-speed digital circuit? (1 Mark)
  - h. Which type of fault is the hardest to detect using traditional stuck-at-fault testing techniques? (1 Mark)
2. Answer the following questions for the circuit shown in Figure 1: (10 Marks)
  - (a) What is the total number of single stuck-at faults in the circuit?
  - (b) How many multiple stuck at faults are possible in the circuit?
  - (c) What is the number of checkpoints in the circuit?
  - (d) Derive the equivalence collapsed set of faults. List all faults that remain after equivalence collapsing.
  - (e) Derive the dominance collapsed set of faults. List all faults that remain after equivalence and dominance collapsing.

 


Figure 1

3. For the circuit in Figure 1, (5 Marks)
 

Perform Deductive Fault Simulation and determine all faults that would be detected at the output z by the test pattern  $x_1 x_2 x_3 x_4 = \{1 \ 1 \ 1 \ 0\}$ . Clearly show the fault lists associated with each signal.

4. For the circuit in Figure 2:

(10 Marks)

- Perform **Concurrent fault simulation** to determine all the faults that would be detected by the test pattern  $abcde=10110$ .
- For the same test pattern as in part a, perform **critical path tracing** and list the critical paths of the circuit (you might need to figure out if a stem is critical through analysis).
- Determine all faults detected using critical path tracing.

 


Figure 2